

# ADVANCED PULSE AND SWITCHING LAB

Studies on RC Low Pass Filter

# Objectives

2

At the end of the module, the student would be able to

- ❑ Explain RC Voltage Dividers
- ❑ Explain RC Circuit as a Low Pass Filter
- ❑ Explain Bode plots

## RC Circuit as Filters

RC circuits can also be used to "filter" a signal waveform, changing the relative amounts of low frequency and high frequency information in their output signals relative to their input signals. There are high-pass filter and low-pass filter and band-pass filter versions of this.

# Impedance of a capacitor

4

$$Z = 1 / \omega C$$


$Z$  = Impedance of Capacitor

$\omega$  = Angular Frequency


$C$  = Capacitance

# RC Voltage Dividers

5

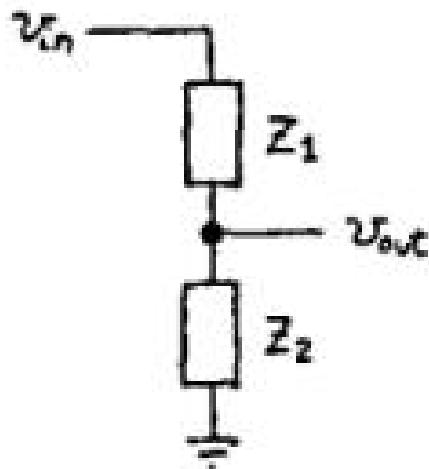

*generalized voltage divider*

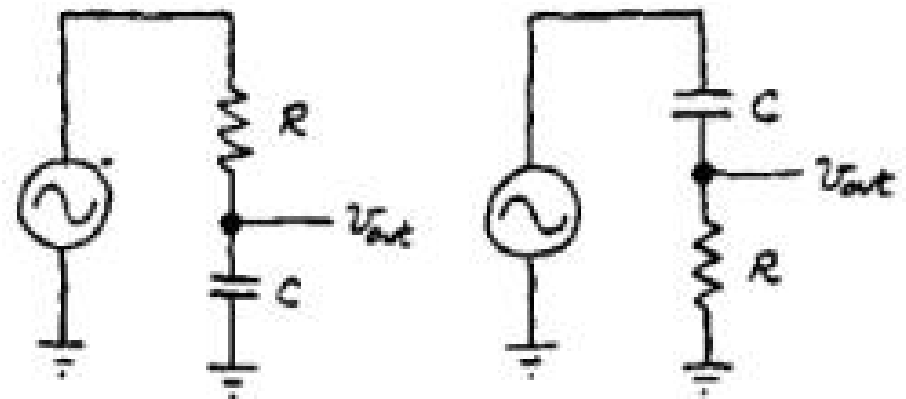


Let us consider RC circuits as voltage dividers to understand how they would perform as 'filters'. Note that  $V_{out} = (Z_2 / Z_1 + Z_2) * V_{in}$ .

In this case – Since  $Z_1$  or  $Z_2$  is dependent upon frequency, the output is dependent upon the frequency of the input waveform.


# RC Voltage Dividers

6

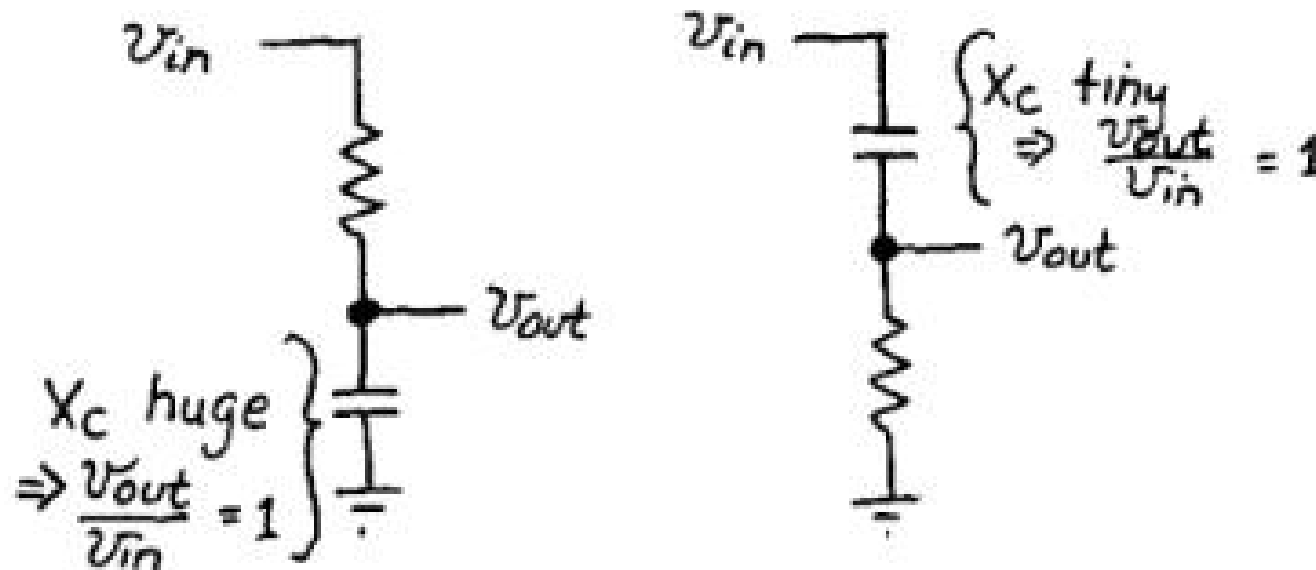

Consider the extreme cases. For the left one— at  $f = 0$ ,  $Z_2 =$  infinite ( huge ), thus all  $V_{out} = V_{in}$ . The lower the 'f', the more  $V_{out}$  will resemble  $V_{in}$ . Thus this one easily passes lower frequency signals through.


# RC Voltage Dividers

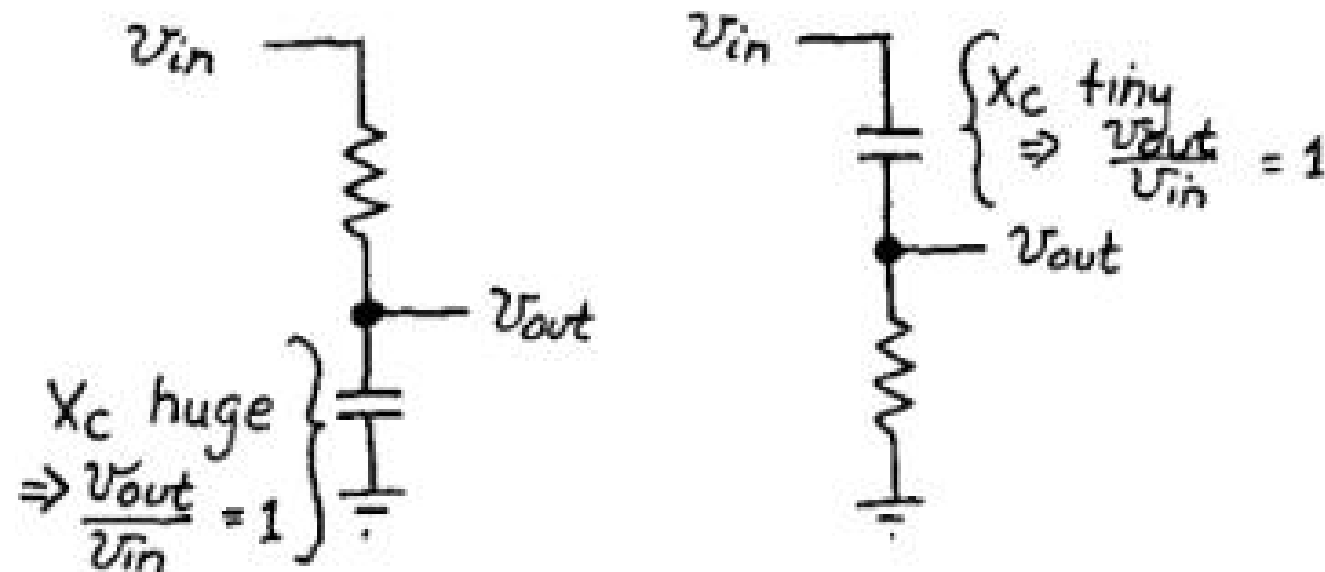

For the right one – at  $f = \text{very high}$ ,  $Z_1 = \text{very small}$ , thus all  $V_{out} = V_{in}$ . The higher the 'f', the more  $V_{out}$  will resemble  $V_{in}$ . Thus this one easily passes higher frequency signals through.

# RC Voltage Dividers


8

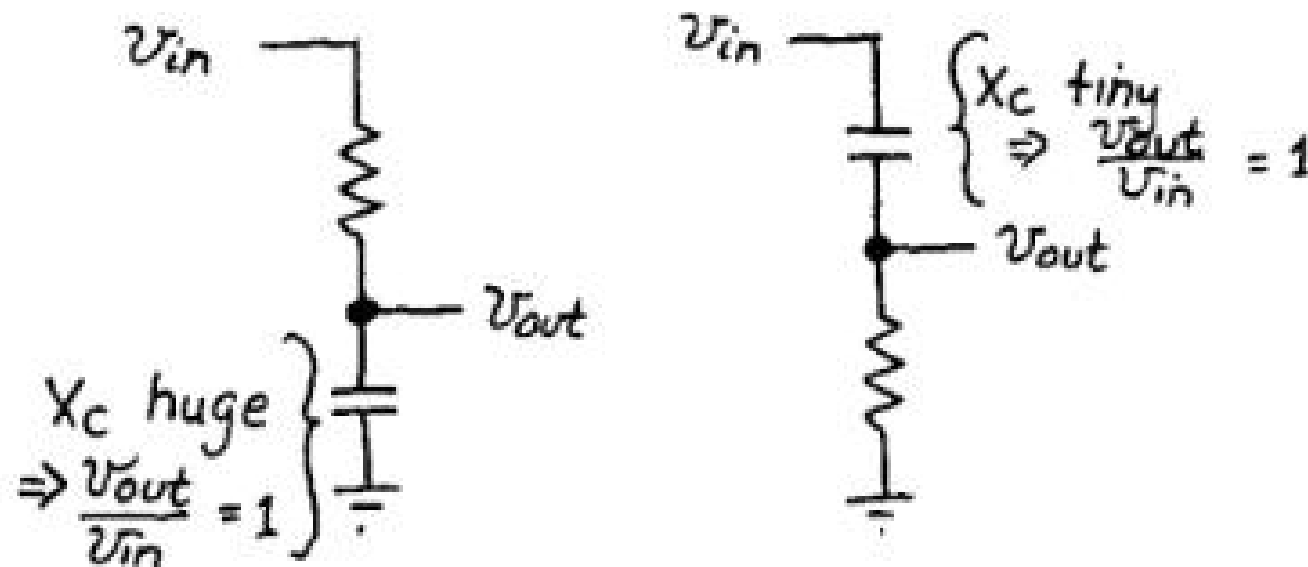

Now let us determine, where the output turns the corner in each case. We will call this 'corner', where the output is 3db less than the input. This is henceforth called the '3db' point. Let us look at how the  $V_{out}/V_{in}$  ratio will change wrt frequency for each now. The plot of this ratio tells us if the circuit behaves as a high pass or as a low pass filter.





# Low Pass Filter

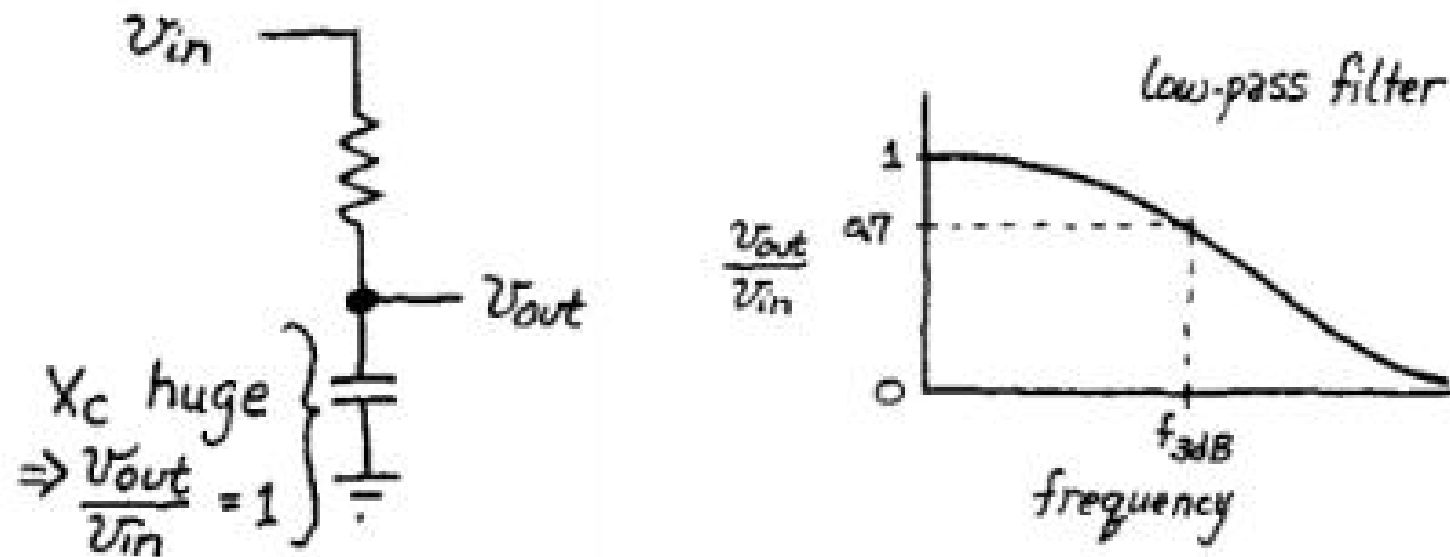

As frequency increases, the impedance of the capacitor (  $Z_2$  ) decreases, thus reducing the  $V_{out}$  (  $= ( Z_2/R + Z_2) * V_{in}$  ). At very high frequency, impedance  $Z_2 =$  very tiny thus forcing  $V_{out}$  to be nearly 0. The '3db' point is given by  $f_{3db} = 1/(2\pi R * C)$ .

# High Pass Filter



10

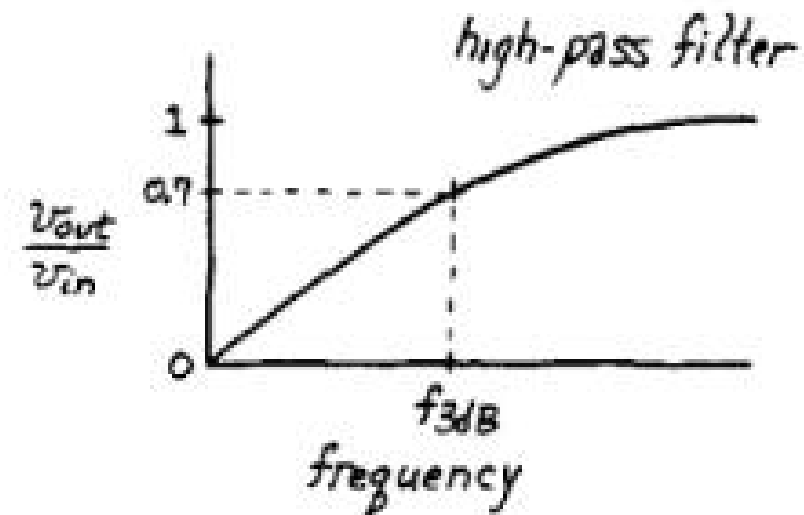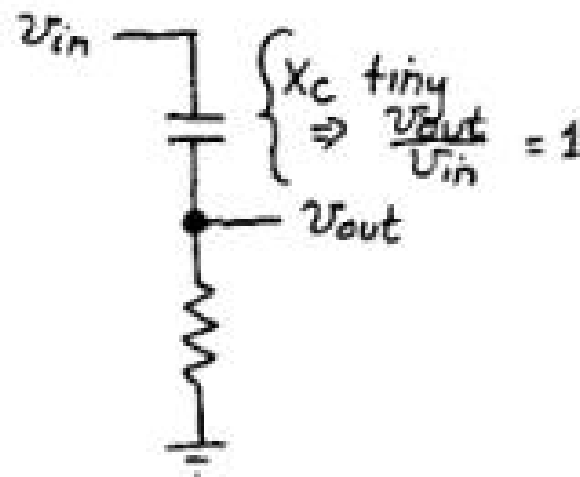

As frequency increases, the impedance of the capacitor decreases, thus increasing the  $V_{out}$  ( $= (R/Z_1 + R) \cdot V_{in}$ ). At very high frequency, impedance  $Z_1 =$  very tiny thus making  $V_{out}$  to be nearly equal to  $V_{in}$ . The '3db' point is given by  $f_{3db} = 1/(2\pi R \cdot C)$ .

# Bode Plots

11

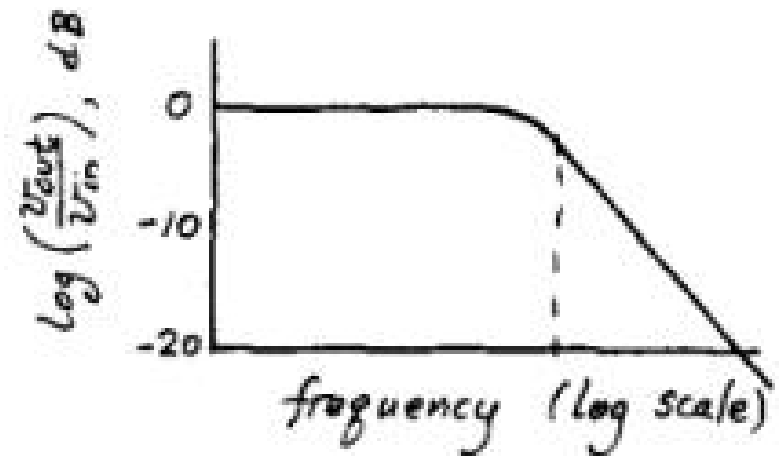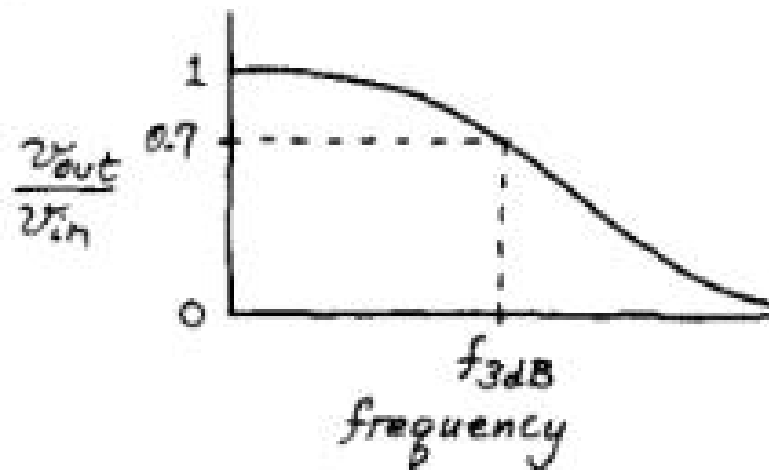

We have been plotting 'linear' plots – Gain (  $V_{out}/V_{in}$  ) vs Frequency. Ideally both the axis are compressed and expressed in the log scale. This is known as 'bode-plots'.

12

## RC as Low Pass filter

# Conclusion

The circuit produces its greatest response at DC. As the frequency is increased, the response drops. Finally, the response drops to zero.

The RC circuit passes 'low' frequencies fairly well, but attenuates 'high' frequencies.

So, we can conclude that RC circuit acts a low-pass filter (LPF).

# Example Frequency Response of RC Low Pass Filter

14

