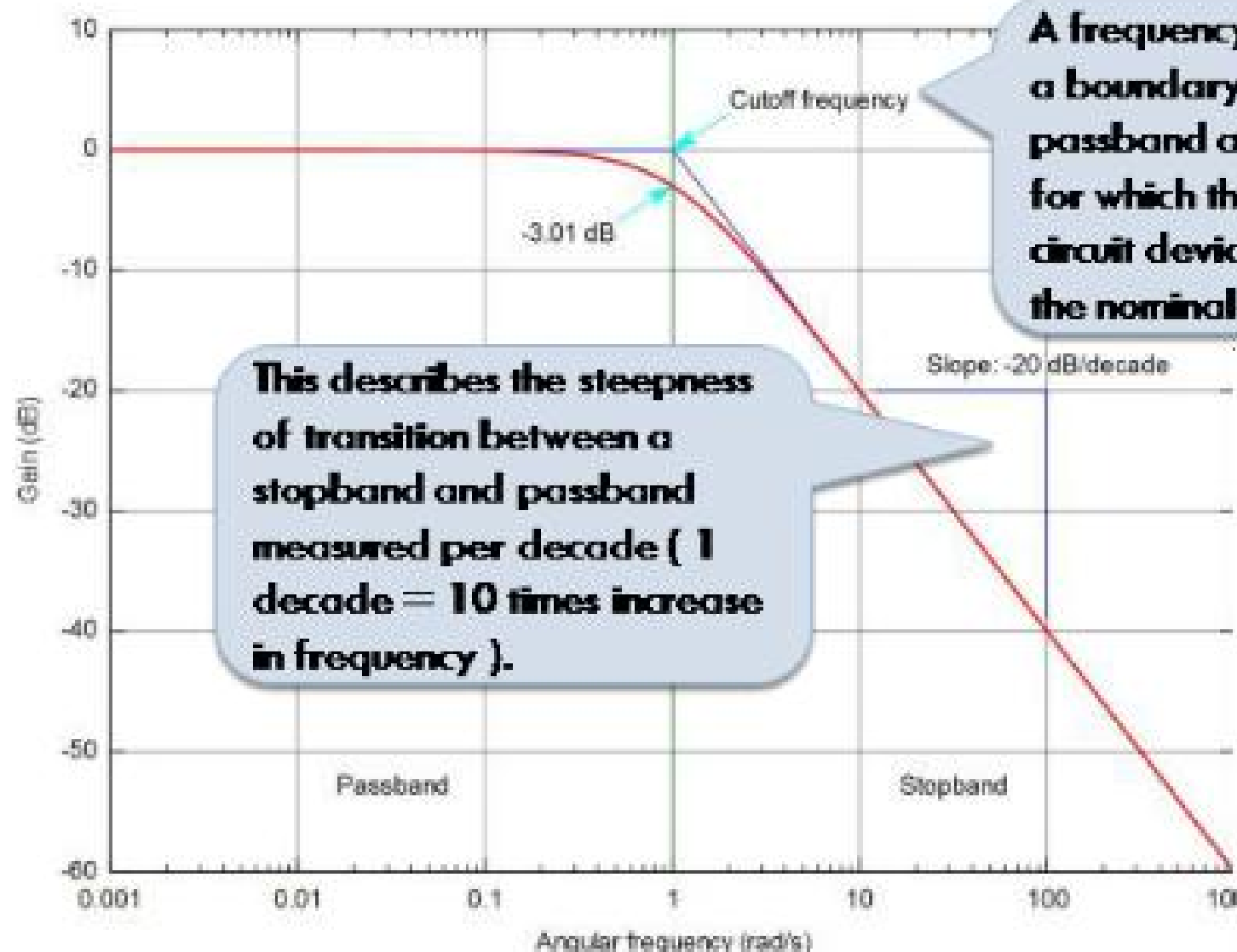


# ADVANCED PULSE AND SWITCHING LAB

Studies on RC Low Pass Filter

# Example Frequency Response of RC Low Pass Filter

2




A frequency characterizing a boundary between a passband and a stopband for which the output of the circuit deviates 3 dB from the nominal passband value.

This describes the steepness of transition between a stopband and passband measured per decade ( 1 decade = 10 times increase in frequency ).
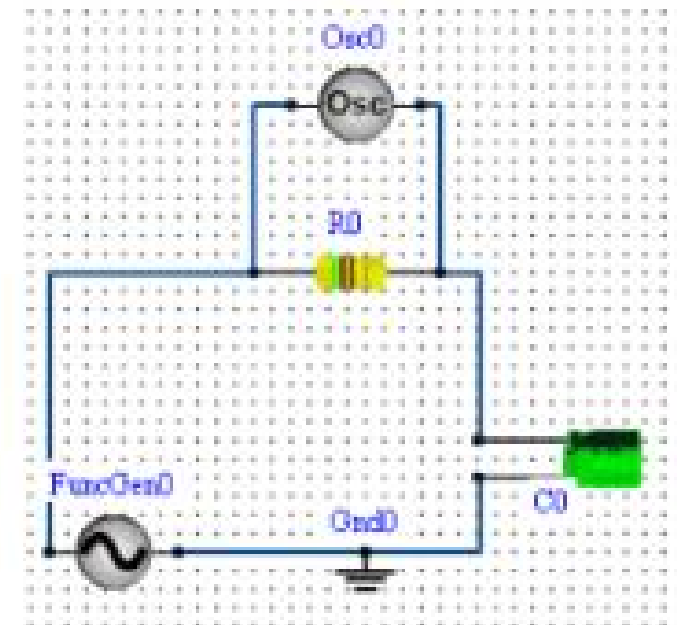
# Experiment Frequency - Response of RC circuit ( Low Pass Filter )

3

- ☐ Drag a function generator and Oscilloscope from the 'Basic' Panel.
- ☐ Drag a Resistor and Capacitor.
- ☐ Construct the circuit as below take  $R = 509 \text{ ohm}$  and  $C = 2 \mu\text{F}$ .
- ☐ Connect the function generator and oscilloscope as shown below.
- ☐ Connect the ground of the circuit.



# Experiment Frequency - Response of RC circuit ( Low Pass Filter )


4

For the function generator select sine wave, and Amplitude 2V. In the Function generator, vary the frequency from 0 Hz to 1 KHz in steps of 100 Hz. For each time, note the peak amplitude of the 2 channels in the scope.



# Experiment Frequency - Response of RC circuit ( Low Pass Filter )

5

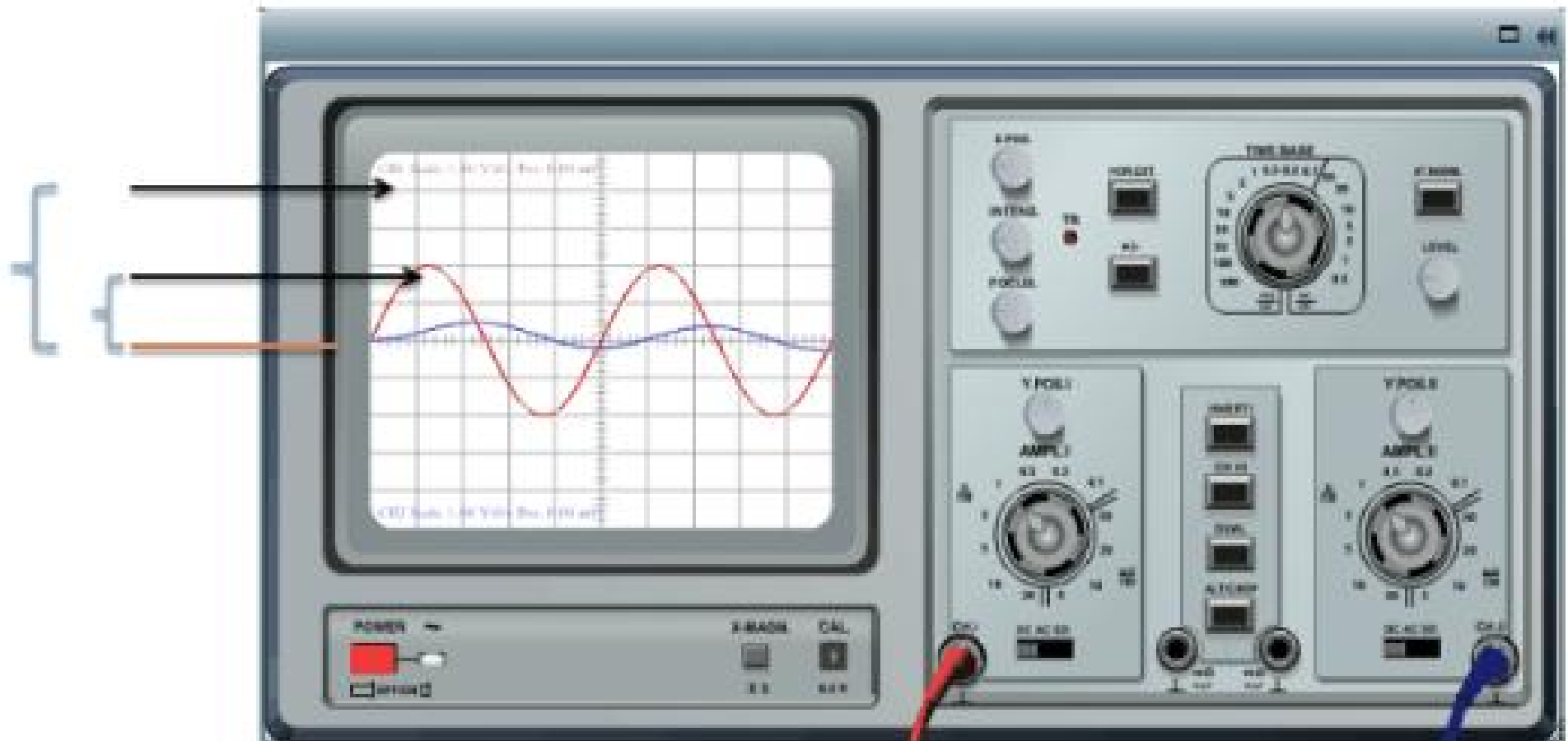

Note the PEAKS of CH1 and CH2 from Oscilloscope

# Experiment Frequency - Response of RC circuit ( Low Pass Filter )

6



Note the readings of  $V_{out}$ ,  $V_{in}$  and frequency over the frequencies and plot a bode graph (  $20 \log(\text{Gain})$  vs frequency ). Observe the '3db' cut off point in the bode plot.

$V_{in}$ ( V )	$V_{out}$ ( V )	Freq ( Hz )	Gain ( $V_{out}/V_{in}$ )	$20\log(\text{Gain})$
2	2	0	1	0
2		100	.	.
2		200	.	.
2		300	.	.
2		400	.	.
...	...	...	...	...
2		1000	.	.
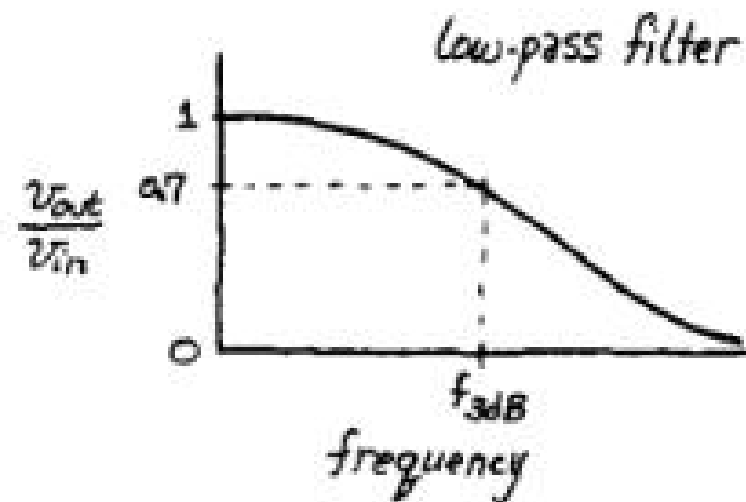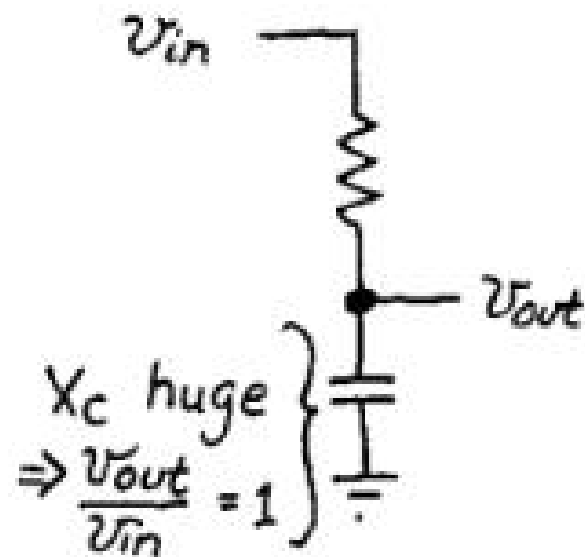
# Experiment Frequency - Response of RC circuit ( Low Pass Filter )

7

Confirm that the circuit indeed is passing lower frequencies and blocking higher frequencies.



8

Is there an easier way of doing this ?

Indeed there is – a way to perform simulations in frequency domain.



# Experiment Frequency - Response of RC circuit ( Low Pass Filter )

9

Construct the circuit as before, take  $R = 500 \text{ ohm}$  and  $C = 2\mu\text{F}$ . For the function generator select sine wave, and Amplitude 2V. In the simulation properties, select 'Frequency Domain Analysis' and vary the frequency from 0 Hz to 1 KHz in steps of 100 Hz. Click on 'Run simulation'.




Freq Domain Analysis ▾

Low Frequency	0	Hz ▾
High Frequency	1	KHz ▾
Step Increment	100	Hz ▾

Advanced ☐

# Experiment Frequency - Response of RC circuit ( Low Pass Filter )

10

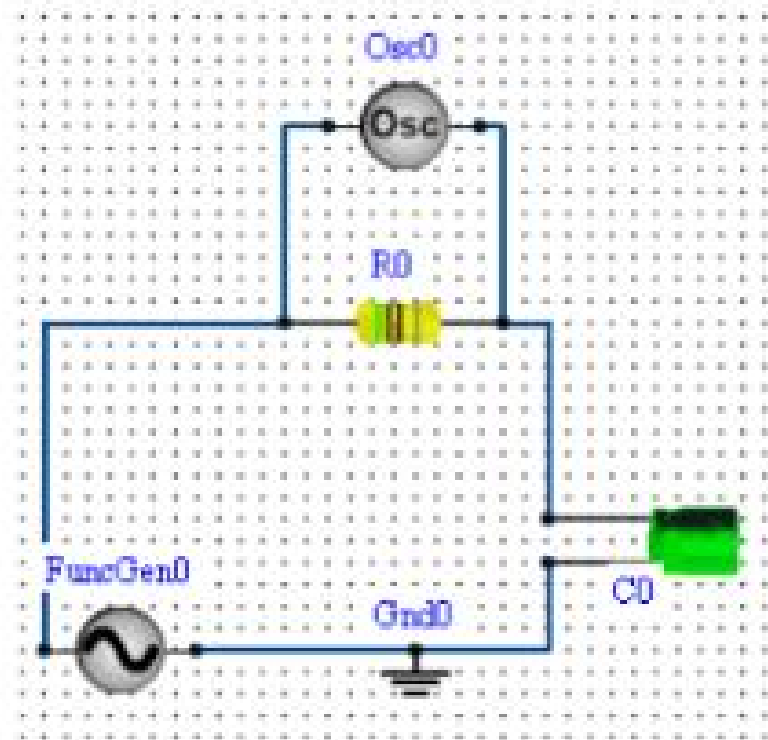

# Experiment Frequency - Response of RC circuit ( Low Pass Filter )

11

Click on the 'Data Analyzer' to see the results. Plot both the voltages (  $V_{in}$  and  $V_{out}$  ) wrt Frequency. We can see that the lower frequencies are passed while the higher frequencies are not passed.



# Experiment Frequency - Response of RC circuit ( Low Pass Filter )

12


Let us now plot the  $V_{out}/V_{in}$  vs frequency and see the results and find out the '3db' point. Click on 'Add Equations' and add the Gain as an equation of  $V_{out}/V_{in}$ . Run simulation again and click on 'Data Analyzer'.


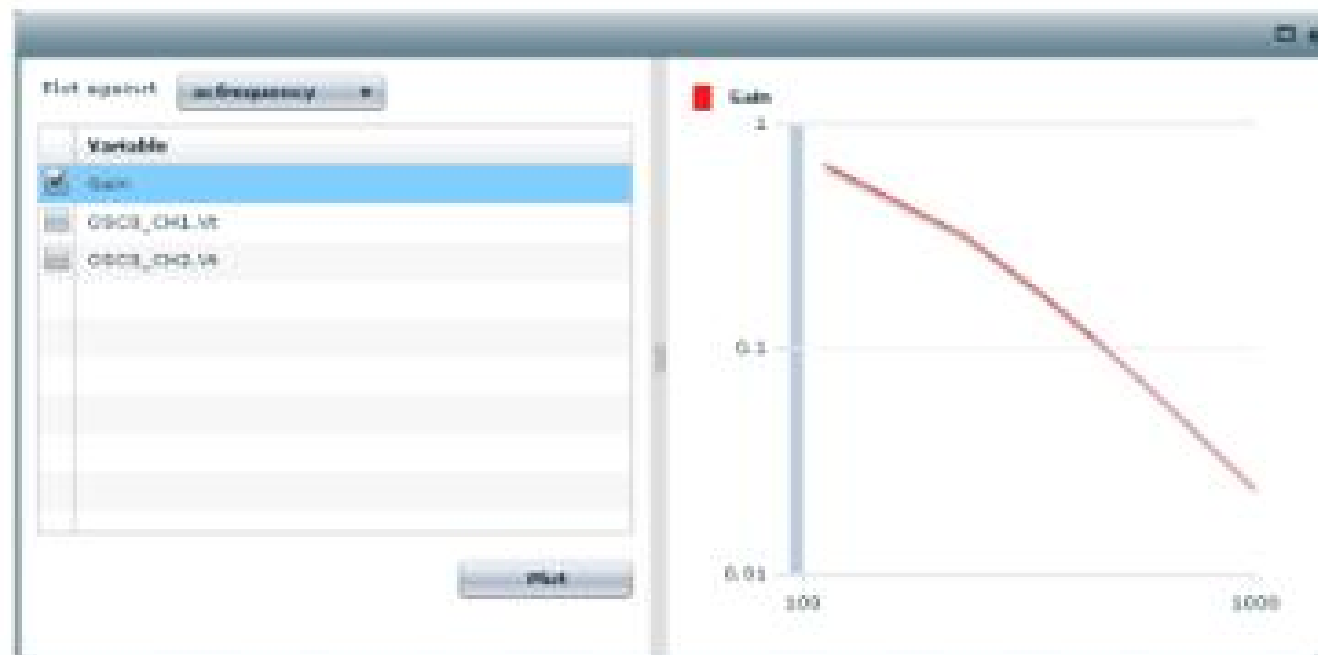
# Experiment Frequency - Response of RC circuit ( Low Pass Filter )

13

On the Data Analyzer, plot Gain vs Frequency and Select the Log scale for both X and Y axis to see the bode-plot. Select the full frequency range for the X axis.




The '3db' or the turning point can now be mapped in the plot.
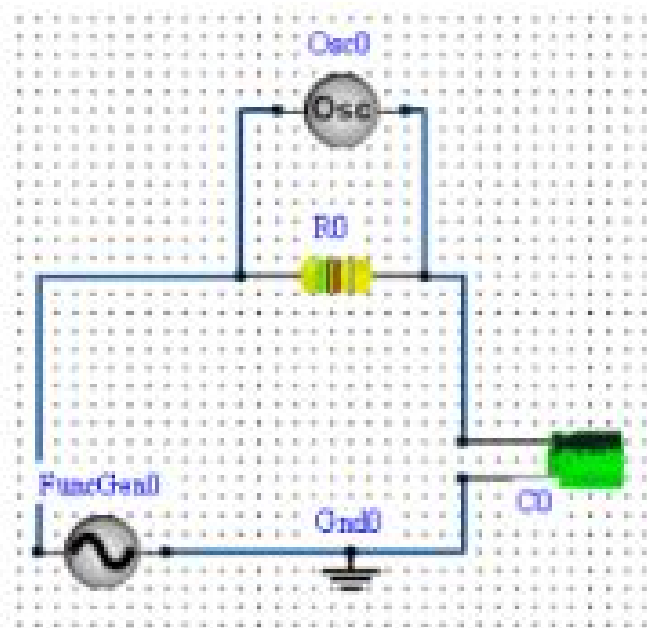
# Exploratory : RC circuit ( Low Pass Filter )

14


Having measured the 3db point, let us try and understand how the 3db point changes with change in Resistor and change in Capacitor.


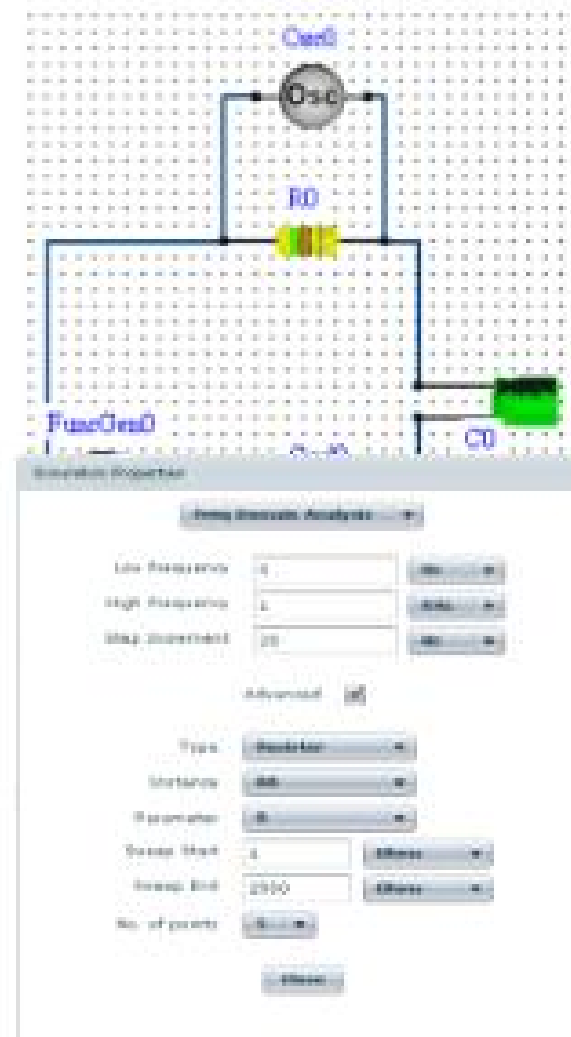
# Exploratory : RC circuit ( Low Pass Filter )

15


- ☐ Construct the circuit as before.
- ☐ In the simulation properties, select 'Frequency Domain Analysis' and vary the frequency from 0 Hz to 1 KHz in steps of 100 Hz.
- ☐ Click Advanced and vary the resistance from 0 Ohms to 2500 Ohms.
- ☐ Run simulation.


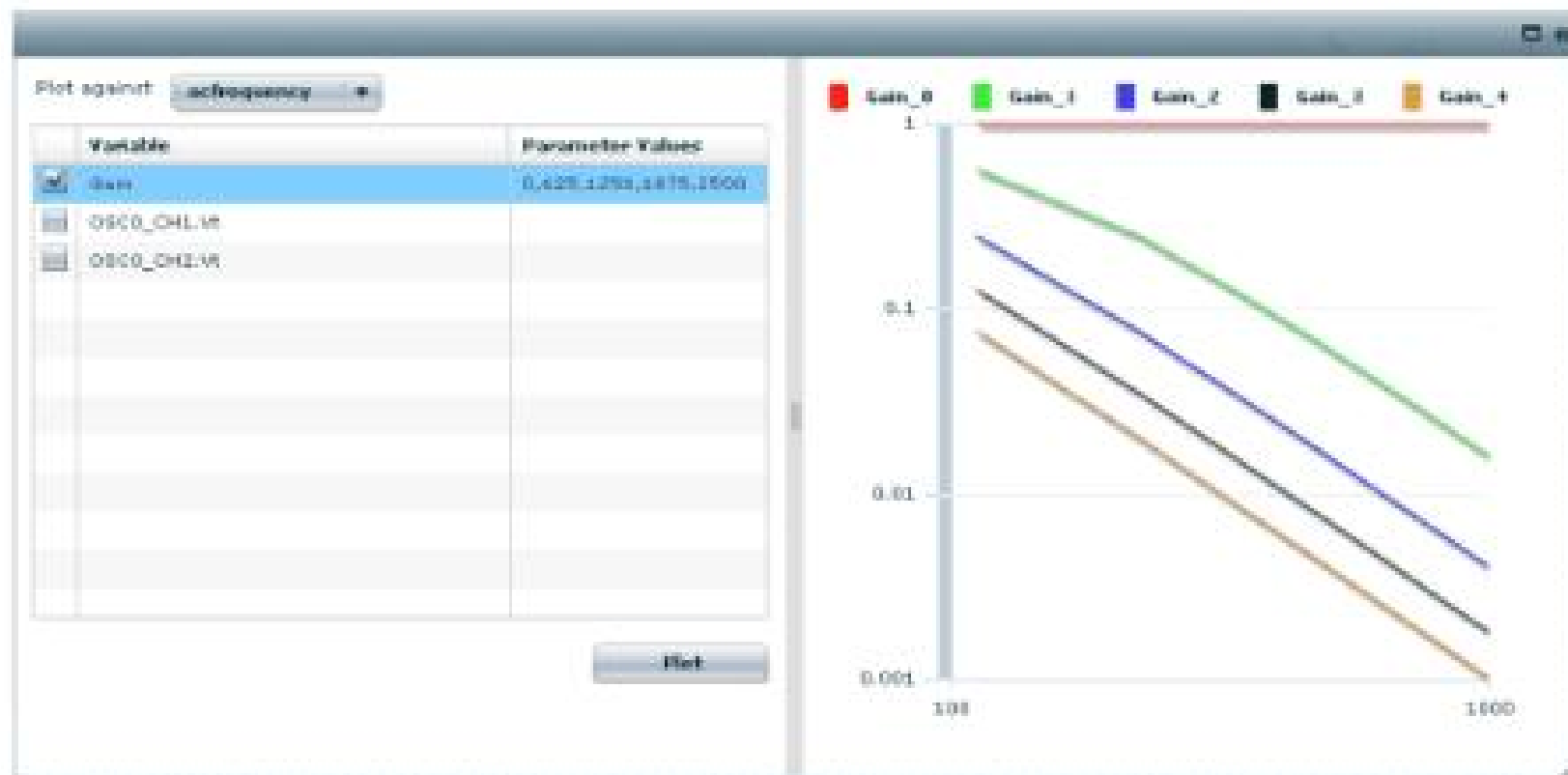
# Exploratory : RC circuit ( Low Pass Filter )

16

Click on Data Analyzer to view the change in 3db point. We can see that 3db point is inversely proportional to change in R.





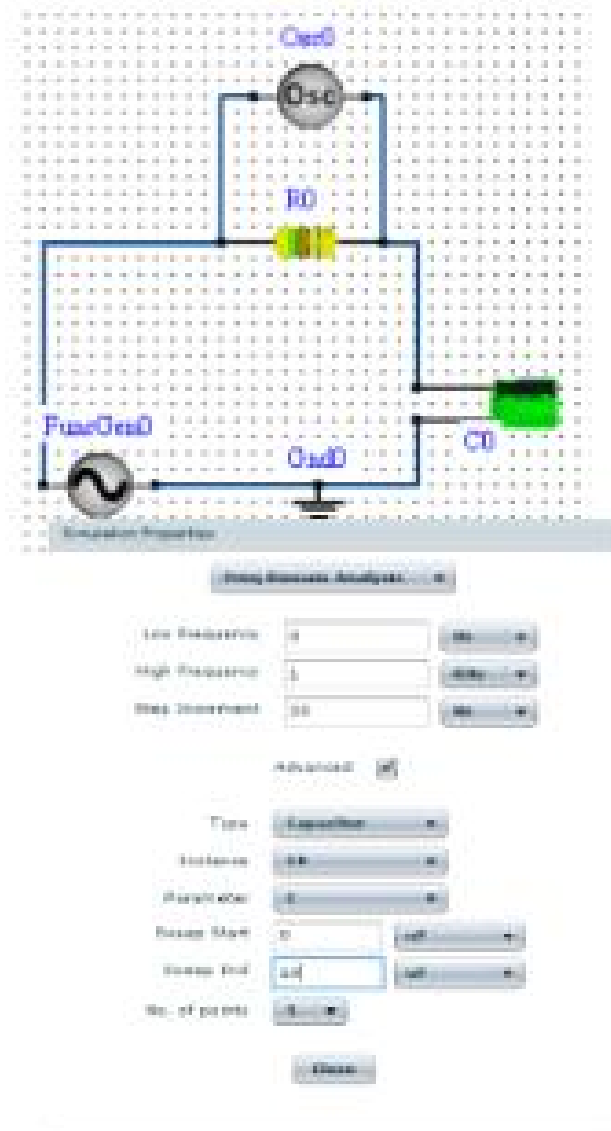
# Exploratory : RC circuit ( Low Pass Filter )

17

- ☐ Let us now vary the capacitance.
- ☐ In the simulation properties, select 'Frequency Domain Analysis'
- ☐ Vary the frequency from 0 Hz to 1 KHz in steps of 100 Hz.
- ☐ Click Advanced and vary the Capacitance from 0 F to 10  $\mu$ F.
- ☐ Run simulation.



# Exploratory : RC circuit ( Low Pass Filter )

18

Click on Data Analyzer to view the change in 3db point. We can see that 3db point is inversely proportional to change in C.

